

# Debugging the DCDCbuck\_Rev10 Board

**Abstract.** This document gives some advice on what to do when a DC/DC buck board is not working properly.

## 1 Introduction and Contents

Sometimes we see that a PCB is not working properly. What actions can be taken to debug the board?

You have to understand the functionality of the board in order to be able to evaluate voltages and waveforms.

## 2 Debugging the DCDCbuck Board

### 2.1 System Setup

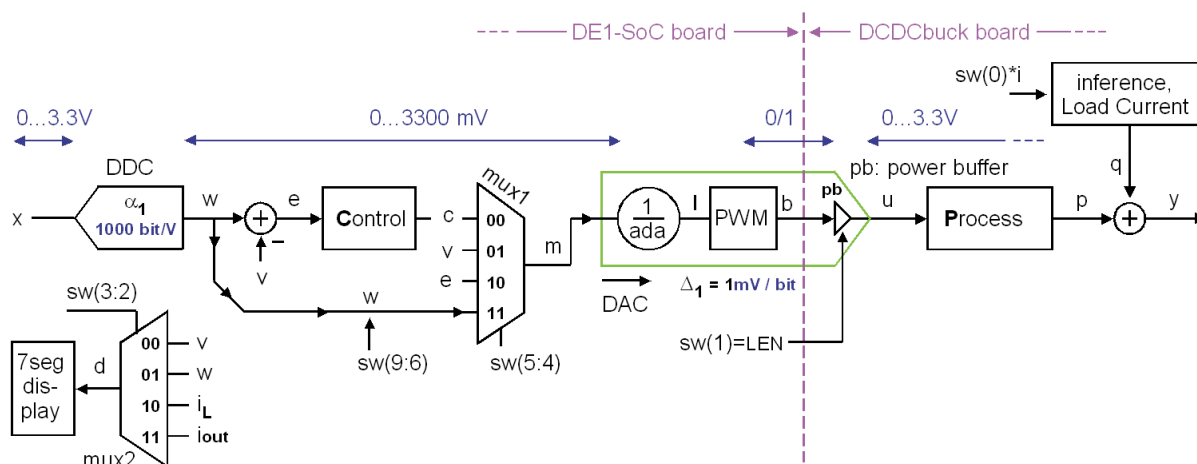


Fig. 2.1: The DC/DC buck converter setup.

Fig. 2.1 illustrates the top-level schematics of the DC/DC controller and illustrates the functionality of its switches:

- sw (9 : 6)** allow to set 15 different reference voltages in mV on signal *w* ("wanted"), setting "1111" refers to a reference voltage delivered by the hard processor system (HPS).
- sw (5 : 4)** take a decision about which signal is used as input to the PWM-DAC.
- sw (3 : 2)** take a decision about which signal is shown on the 7-segment display.
- sw (1)** decides on synchronous ('1') or asynchronous ('0') operation.
- sw (0)** enables a load current of 1A to be switched on ('1').

Set an output voltage of some  $100\text{mV} > 1\text{V}$ , e.g. 1250V using **sw (9 : 6)** "0000".

To debug the digital part of the DCDCbuck board, it makes sense to open the feedback loop, bypass the controller and put reference *w* directly at the input of the PWM modulator. To so, set the following switches (solutions see below):

**sw ( \_\_\_\_\_ ) = \_\_\_\_\_ .**

Display the output voltage *v* measured by ADC *LTC2308* on the 7-segment display

**sw ( \_\_\_\_\_ ) = \_\_\_\_\_ .**

Set synchronous operation and load current off:

**sw ( \_\_\_\_\_ ) = \_\_\_\_\_ .**

in summary, the overall switch setting is

**sw (9 : 0) = \_\_\_\_\_ .**

**Solutions to chapter 2.1:** Setting of switches for this test:

To debug the digital part of the DCDCbuck board, it makes sense to open the feedback loop, bypass the controller and put reference  $v$  directly at the input of the PWM modulator. To so, set the following switches (solutions see below):

$sw(5:4) = 11$

Display the output voltage  $v$  measured by ADC *LTC2308* on the 7-segment display

$sw(3:2) = 00$

Set synchronous operation and load current off:


$sw(1:0) = 10$

in summary, the overall switch setting is

$sw(9:0) = 0000110010$

## 2.2 Schematics for Testing the LM27222

### 2.2.1 First Tests

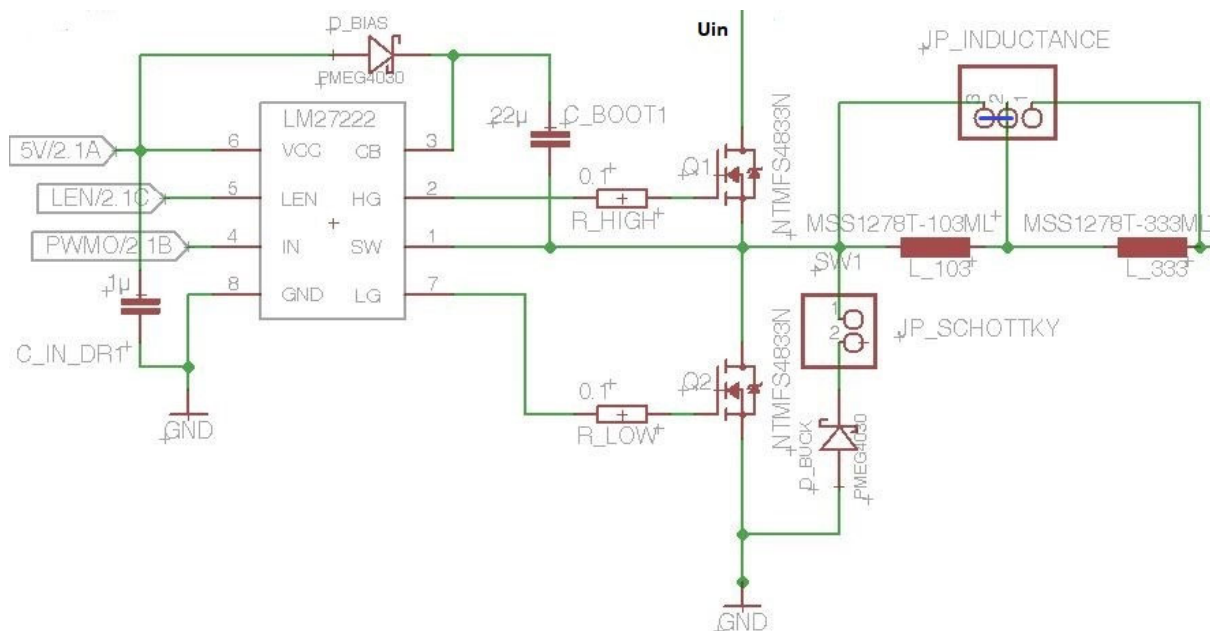


**Fig. 2.2.1:** The DC/DC buck converter schematics for LM27222 tests.

Only hold the board by the side edges. If you must touch devices on the board, do so with clean fingers and avoid touching conductive parts such as wireline pins. This is because human skin is covered in a layer of sweat, salt and fat. This can cause leakage currents between conductive elements.

1. Apply light bending stress to the board. This must not impair its function
2. Try pushing larger components back and forth a little. They should not wobble and these forces should not affect the functionality of the board.
3. During normal operation, no device should get so hot that you cannot touch it. Check the board under an infrared camera or touch critical devices carefully with clean fingers.

## 2.2.2 Checking voltages and signals with probe and Oscilloscope

**Fig. 2.2.2:** Probe to be connected to the oscilloscope with a BNC plug. Be aware, that many probes have a built-in 1:19 voltage divider.

 

Use a probe as illustrated in Fig. 2.2.2, which is attached to your oscilloscope. Be careful to not cause short circuits between neighboring pins when touching LM27222 I/O pins with the probe.

Identify the *LM27222* chip on your DCDCbuck board. Identify pin 1 ... pin 8 using the datasheet [LM27222].

[LM27222]: [https://www.ti.com/lit/ds/symlink/lm27222.pdf?ts=1667637493881&ref\\_url=https%253A%252F%252Fwww.google.com%252F](https://www.ti.com/lit/ds/symlink/lm27222.pdf?ts=1667637493881&ref_url=https%253A%252F%252Fwww.google.com%252F)

Connect *CH1* of the oscilloscope with pin3 of JP1=gpio\_0 user header of the *DE1-SoC* board. Connect *CH2* of the oscilloscope with pin1 of JP1=gpio\_0 user header of the *DE1-SoC* board. (Check results with Figs. in chapter 2.3.) Verify with a probe at *CH3* that *LM27222*'s ...

- $pin8 = gnd = 0V$  % is the ground pin really connected to ground?
- $pin6 = VCC = 5V$  % is the VCC pin connected to 5V?
- $pin4 = IN = pin6$  % should be identical to pwmo on CH2
- $pin7 = LG == (NOT(pwmo) \text{ AND } LSE)$  % check LG. Note:  $LSE = LEN = sw(1)$
- $pin2 = HG = a_1 \cdot pwmo + a_0$ , whereas  $a_1 > 0$ ,  $a_0 \geq 0$  % check HG
- $pin1 = SW = a_1 \cdot pwmo + a_0$ , whereas  $a_1 > 0$ ,  $a_0 \geq 0$  % check switching node SW
- $pin3 = CB = a_1 \cdot pwmo + a_0$ , whereas  $a_1 > 0$ ,  $a_0 \geq 0$  % check boots-trap node CB

## 2.3 Checking Signals at Pins of LM27222

### 2.3.1 Check Control Signals *pwmo* (IN), Low-Gate (LG), High-Gate (HG)

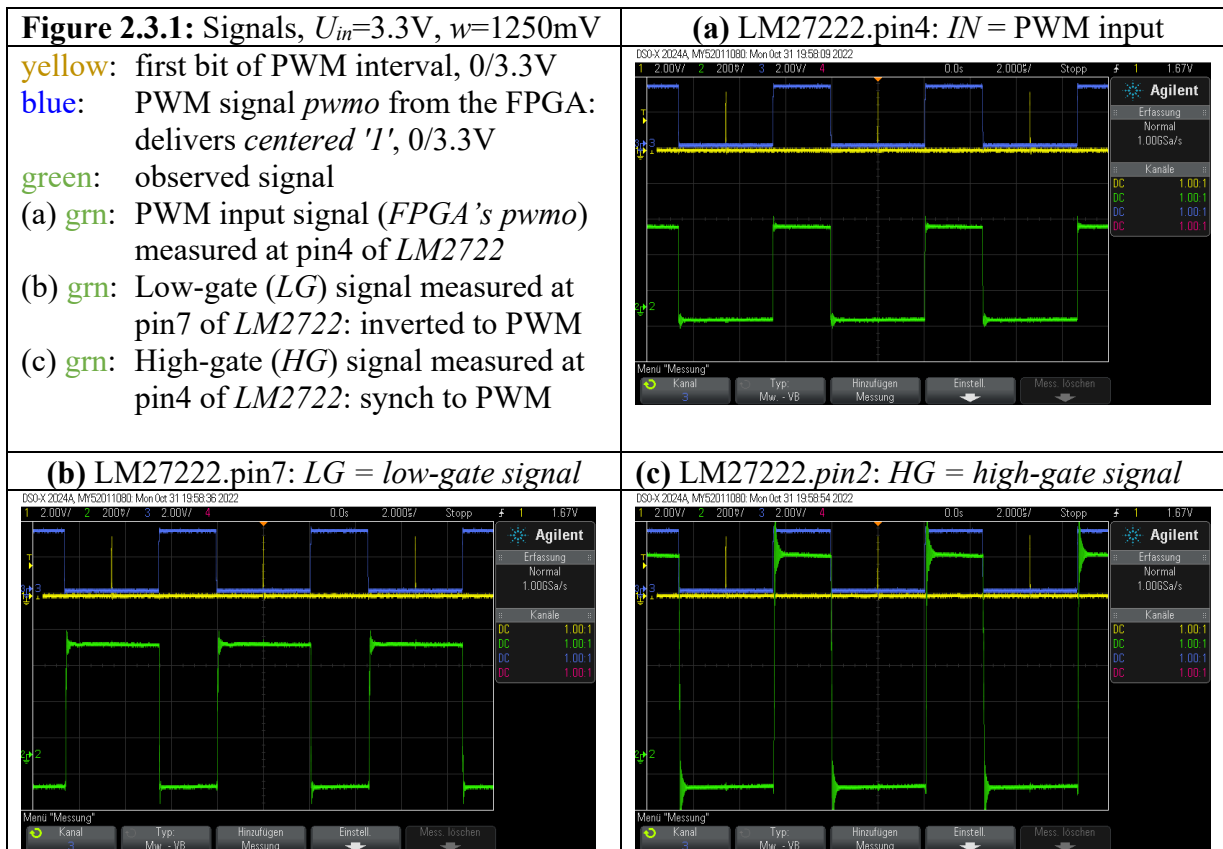


Fig. 2.3.1(a) illustrates, that the PWM signal coming from the *FPGA's* signal *pwmo* (blue) appears on as input on *pin4 = IN* of the *LM27222*. Measure:

**IN = LM27222.pin4 low level = \_\_\_\_\_ , high level = \_\_\_\_\_ .**


Fig.2.3.1(b) illustrates, that the low-gate signal *LG = pin7* is inverted to the PWM input when *sw(1) = '1'*; and *LG = '0'* otherwise.

**LG = LM27222.pin7 low level = \_\_\_\_\_ , high level = \_\_\_\_\_ .**

Fig.2.3.1(c) illustrates, that the high-gate signal *HG = pin2* is in phase with the PWM input signal, but has a strongly amplified *High* level.

**HG = LM27222.pin2 low level = \_\_\_\_\_ , high level = \_\_\_\_\_ .**
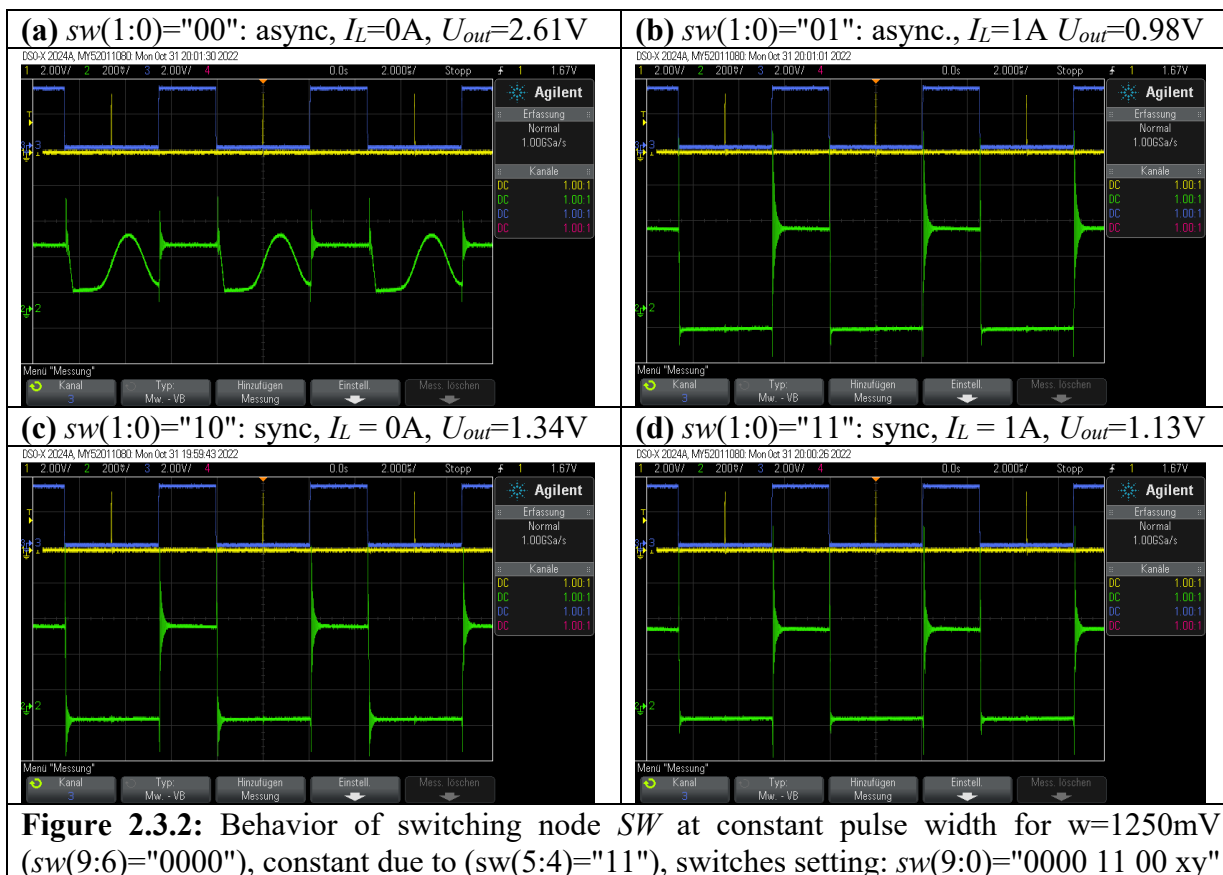
### 2.3.2 Check Behavior of Switching Node $SW$



In the following measurements, you may take  $I_{out}$  and  $U_{out}$  from the 7-segment display.

Fig. 2.3.2(a) shows voltage at switching node  $SW$  for async. operat. and  $I_L = 0$ . Measure levels:

(a)  $SW = low = \underline{\hspace{1cm}}$  ,  $high = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

Fig. 2.3.2(b) shows voltage at switching node  $SW$  for async. oper. and  $I_L = 1A$ . Measure levels:

(b)  $SW = low = \underline{\hspace{1cm}}$  ,  $high = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .


Fig. 2.3.2(d) shows voltage at switching node  $SW$  for sync. oper. and  $I_L = 0A$ . Measure levels:

(c)  $SW = low = \underline{\hspace{1cm}}$  ,  $high = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

Fig. 2.3.2(d) shows voltage at switching node  $SW$  for sync. oper. and  $I_L = 1A$ . Measure levels:

(d)  $SW = low = \underline{\hspace{1cm}}$  ,  $high = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

### 2.3.3 Check Behavior of Bootstrap Node *CB*

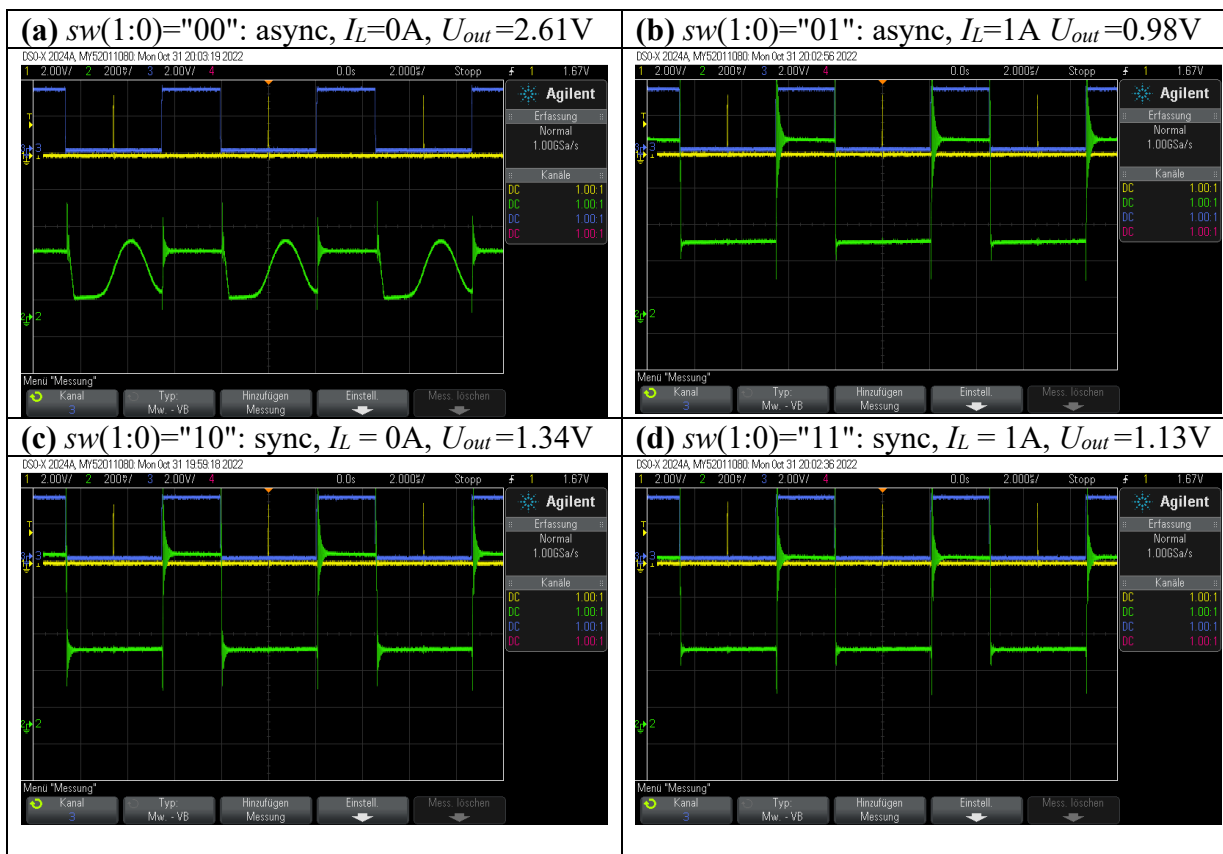

**Figure 2.3.3:** Behavior of bootstrap node *CB* at constant pulse width set for  $U_{out}=1250\text{mV}$  (by  $sw(9:6)=""0000""$ ) at  $U_{in}=3.3\text{V}$ , pulse-width is constant due to ( $sw(5:4)=""11""$ ), total switches setting is:  $sw(9:0)=""0000\ 11\ 00\ xy""$

In the following measurements, you may take  $I_{out}$  and  $U_{out}$  from the 7-segment display.

Fig. 2.3.2(a) shows voltage at bootstrap node *CB* for async. operat. &  $I_L=0$ . Measure levels:

(a)  $CB = \text{low} = \underline{\hspace{1cm}}$  ,  $\text{high} = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

Fig. 2.3.2(b) shows voltage at bootstrap node *CB* for async. operat. &  $I_L=1\text{A}$ . Measure levels:

(b)  $CB = \text{low} = \underline{\hspace{1cm}}$  ,  $\text{high} = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

Fig. 2.3.2(c) shows voltage at bootstrap node *CB* for sync. operat. &  $I_L=0$ . Measure levels:


(c)  $CB = \text{low} = \underline{\hspace{1cm}}$  ,  $\text{high} = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

Fig. 2.3.2(d) shows voltage at bootstrap node *CB* for sync. operat. &  $I_L=1\text{A}$  Measure levels:

(d)  $CB = \text{low} = \underline{\hspace{1cm}}$  ,  $\text{high} = \underline{\hspace{1cm}}$  ,  $I_{out} = \underline{\hspace{1cm}}$  ,  $U_{out} = \underline{\hspace{1cm}}$  .

### 2.3.4 Computing DC Resistor $R_D$

(a) System setup

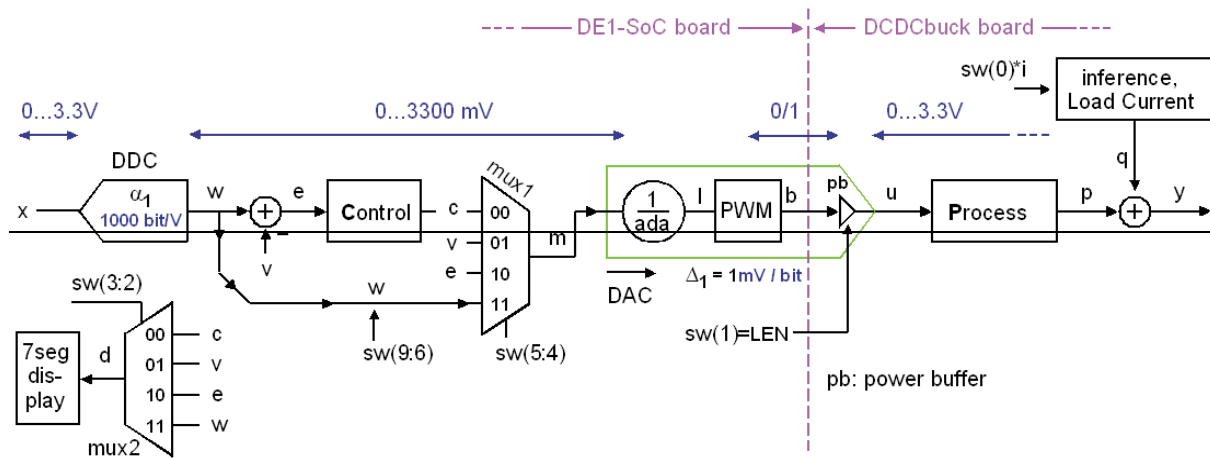

(b) RLC low-pass forming the process

 


Fig. 2.3.4:

(a) System setup,

(b) Assuming the RLC lowpass to be driven by an inner DC source  $U_{int,dc}$  and an serial AC source  $U_{int,av}$ .

According to Fig. 2.3.4 we model the PWM driver as DC source  $U_{int,dc}$  plus AC source  $U_{int,ac}$ . The effect of the AC source is largely eliminated by the RLC low-pass filter, so that we can measure  $U_{int,dc}$  as average output voltage at zero load current. After switching on the load current  $I_{out}$ , the average output voltage  $U_{out,av}$  decreases by  $R_D \cdot I_{out}$ .

Set  $sw = "0000 11 00 10"$  to get  $w=1250mV$ , fixed pulse-width and synchronous operation.

Measure at  $sw(0)='0'$  :  $U_{int,dc} = U_{out,av,OFF} = \underline{\hspace{2cm}} mV$ ,  $I_{out,OFF} = \underline{\hspace{2cm}} mA$ ,

Measure  $sw(0)='1'$  :  $U_{out,av,ON} = \underline{\hspace{2cm}} mV$ ,  $I_{out,ON} = \underline{\hspace{2cm}} mA$ ,

Compute  $R_D(w=1250mV) = \frac{U_{int,DC} - U_{out,av}}{I_{out,ON} - I_{out,OFF}} = \underline{\hspace{2cm}}$ .

Hint:  $R_D$  should be in the range of 140...160 mΩ.

Measured on board # 06 of type DCDCbuckRev10.02 on 18.11.2022

Measure at  $sw(0)='0'$  :  $U_{int,dc} = U_{out,av,OFF} = 1332 mV$ ,

$I_{out,OFF} = 10 mA$ ,

Measure  $sw(0)='1'$  :  $U_{out,av,ON} = 1194 mV$ ,

$I_{out,ON} = 970 mA$ ,

Compute  $R_D(w=1250mV) = (1332-1194) / (970-10) = 0,144$



### 2.3.5 Check Behavior for Zero Load Current

Try to explain the voltage bump of node  $SW$  when the high-side power  $FET$  is  $OFF$  in Fig. 2.3.2(a).

Despite  $sw(0)=0$ , a small load current flows. Repeat the measurement of Fig. 2.3.2(a) (with still bypassed controller:  $sw(5:4)=""00""$ ) and remove Jumper  $JP\_Load$ . What happens? Why?

Switch on the control unit:  $sw(5:4)=""00""$ . Switch  $sw(1)$  = synchronous mode briefly ON and OFF again. Observe  $U_{out}$  and  $U(SW)$ . What happens? Explain!

### Solutions to chapter 2.3.4:

Try to explain the voltage bump of node  $SW$  when the high-side power  $FET$  is  $OFF$  in Fig. 2.3.2(a).

1. **Low phase:** In the first moment, when the high-side switch goes to  $OFF$ , the current through the coil is still flowing forward (into capacitor  $C$ ) holding node  $SW$  down.
2. **Positive ramp:** After a while, the charge flows back from  $C$  through  $L$  to node  $SW$ , so that its node voltage rises.
3. **Negative ramp:** A small load current is still flowing, with must be delivered through the coil pulling down again  $U(SW)$ .

Despite  $sw(0)='0'$ , a small load current flows. Repeat the measurement of Fig. 2.3.2(a) (with still bypassed controller:  $sw(5:4)='00'$ ) and remove Jumper  $JP\_Load$ . What happens? Why?  $I_{out} = 0$  now. Nodes  $SW$  and  $U_{out}$  float up to higher voltages.  $PWM$  input pulses are still observed, but no more on nodes  $SW$  and  $CB$  -> the charge pump is dead.

Switch on the control unit:  $sw(5:4)='00'$ . Switch  $sw(1)$  = synchronous mode briefly  $ON$  and  $OFF$  again. Observe  $U_{out}$  and  $U(SW)$ . What happens? Explain!  
Same as above, but no more input pulses coming from  $pwm$  are observed, because now the controller seeks to pull  $U_{out}$  down.

## 3 References

- [1] Texas Instruments, “*LM27222 High-Speed 4.5A Synchronous MOSFET Driver*”, avail.: [https://www.ti.com/lit/ds/symlink/lm27222.pdf?ts=1662800602460&ref\\_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FLM27222](https://www.ti.com/lit/ds/symlink/lm27222.pdf?ts=1662800602460&ref_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FLM27222).
- [2] Linear Technology (today: Analog Devices), “*Low Noise, 500ksp/s, 8-Channel, 12-Bit ADC*”, available: <https://www.analog.com/media/en/technical-documentation/data-sheets/2308fc.pdf>
- [3] Texas Instruments, “*INA240 – 4-V to 80-V, Bidirectional, Ultra-Precise Current Sense Amplifier With Enhanced PWM Rejection*”, available: [https://www.ti.com/lit/ds/symlink/ina240.pdf?ts=1662820015241&ref\\_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FINA240](https://www.ti.com/lit/ds/symlink/ina240.pdf?ts=1662820015241&ref_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FINA240)
- [4] Texas Instruments, “*REF50xx – Low-Noise, Very Low Drift, Precision Voltage Reference*”, available: [https://www.ti.com/lit/ds/symlink/ina240.pdf?ts=1662820015241&ref\\_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FINA240](https://www.ti.com/lit/ds/symlink/ina240.pdf?ts=1662820015241&ref_url=https%253A%252F%252Fwww.ti.com%252Fproduct%252FINA240)