



Getting Started With *DCDCbuck* Board

Prof. Dr. Martin J. W. Schubert, Electronics Laboratory,
OTH Regensburg, Regensburg, Germany

Getting Started With *DCDCbuck* Board

Abstract. This communication presents the *DCDCbuck* converter board, which is used as daughter board to *Terasic's DE1-SoC* board.

1 Introduction

1.1.1 Objectives

This document introduces to the usage of the *DCDCbuck* board, performing DC/DC step-down conversion as daughter board of *Terasic's DE1-SoC* board. With an A/D converter available, the *DCDCbuck* board can also be used with other *DEx* boards with compatible user header, e.g. *DE2*, *DE2-70*, *DE2-115*.

1.2 Assumed Test Environment

1.2.1 *DE1-SoC* Hardware

This document assumes that you are familiar with the *Terasic's* [1] *DE1-SoC* board [2] or a similar *DEx* board with the same general-purpose input/output (GPIO) user header. The version of your *DE1-SoC* board can be identified at [3]. *DE1-SoC* board revisions *F* and *G* differ in a printed company label only. To get this information from the internet, navigate your browser to [4] and download *DE1-SoC_v.5.1.2_HWrevF_SystemCD.zip* [5] or a later version. It contains amongst other things important documents such as *DE1-SoC User Manual* [6] and *Schematic* [7]. On the computer system of OTH Regensburg you will also find the CD on drive K:\Sb\ [8]. Do not use any other manual revision to follow this documentation. The differences may be considerable.

1.2.2 *Quartus II* [9] and *ModelSim* [10] Software Tools

It is assumed that you have *Intel's ModelSim* [10] and *Quartus II 18* [9] software available. To download this freeware for your private PC you have to sign in at *Intel* [11]. At OTH Regensburg's PC pools of faculties *EI* and *IM*, this software is installed. At faculty *EI*, also *Quartus II 8* is installed supporting the older *DE2* boards with *Cyclone II* FPGAs, which are not supported for *Quartus II* versions greater than 13.1.

1.2.3 Use of *VHDL*

The *IEEE standard VHDL Language reference manual* [12] is difficult to read. *Qualis VHDL Quick Reference Card* [13] and *1164 Packages Quick Reference Card* [14] are compact but difficult to understand. Feel free to find your own sources.

VHDL is not case sensitive. In the following, **VHDL KEYWORDS** will be written in **ALL CAPITAL LETTERS** and user defined names in **lowercase letters**. Exception are capitalized initials

used for composed self-made names, e.g. *AddressBus* or *DataBusBitWith*. Self-made data types begin with *t_*, e.g. *t_StateVector*.

1.3 Contents

The **organization** of this document is as follows:

Section **1** is this **introduction**,

Section **2** presents the *DCDCbuck* board **hardware**,

Section **3** suggests some **tests and basic characterization** methods of the *DCDCbuck* board,

Section **4** draws relevant **conclusion** and

Section **5** offers **references**.

1.4 Acknowledgements

The author would like to thank *Terasic Technologies* [1] for authorization to use copies of *Terasic* documentation for *DEI-SoC* boards for teaching purposes.

2 The DCDCbuck Daughter Board Hardware


 



Fig. 2.1: DE1-SoC board (left) carrying the DCDCbuck daughter board (right). The orange wire connects the input of the DE1-SoC on-board's ADC (LTC2308) channel 0 with the DCDCbuck board's output voltage.

Fig. 2.2:
Eagle [18] Layout of DCDCbuck board.

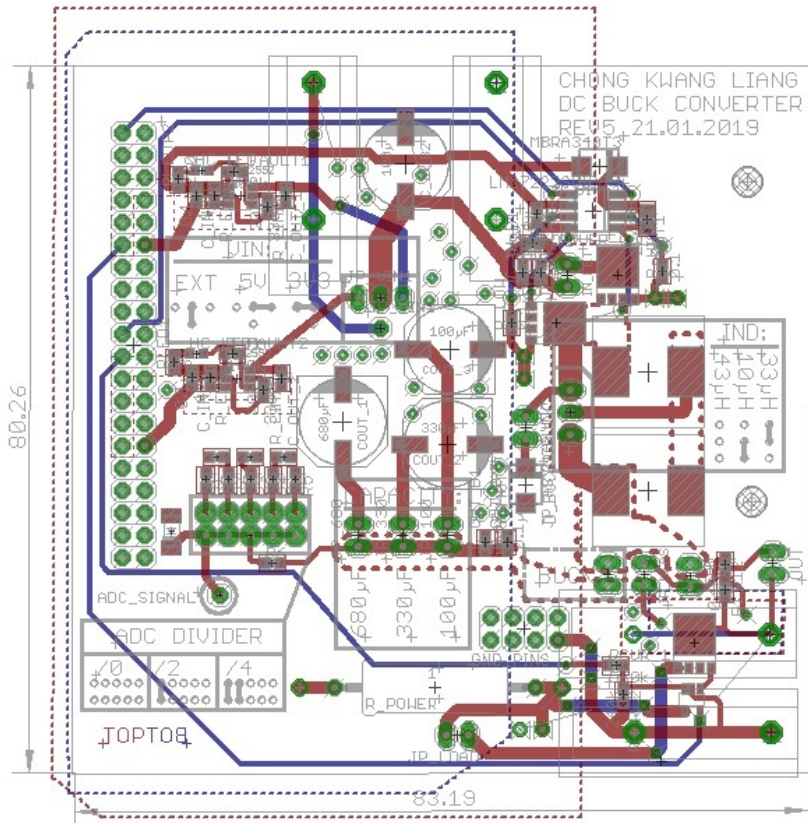- Brown:** top layer metal wires
- Blue:** bottom layer metal wires
- Green:** vias & contacts.



(a) View 1: DC/DC buck converter

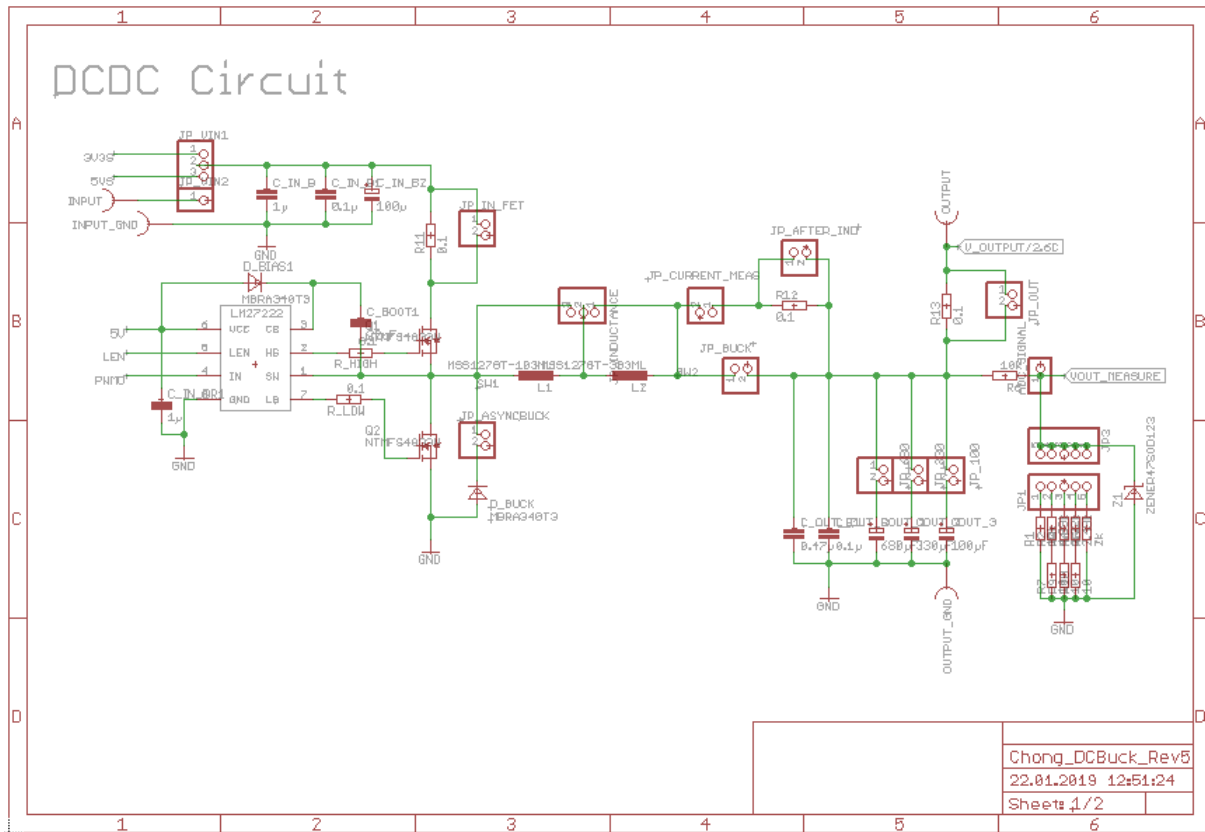

(b) View 2: 5V and 3.3V input current limiters, user and ground header, load current circuit

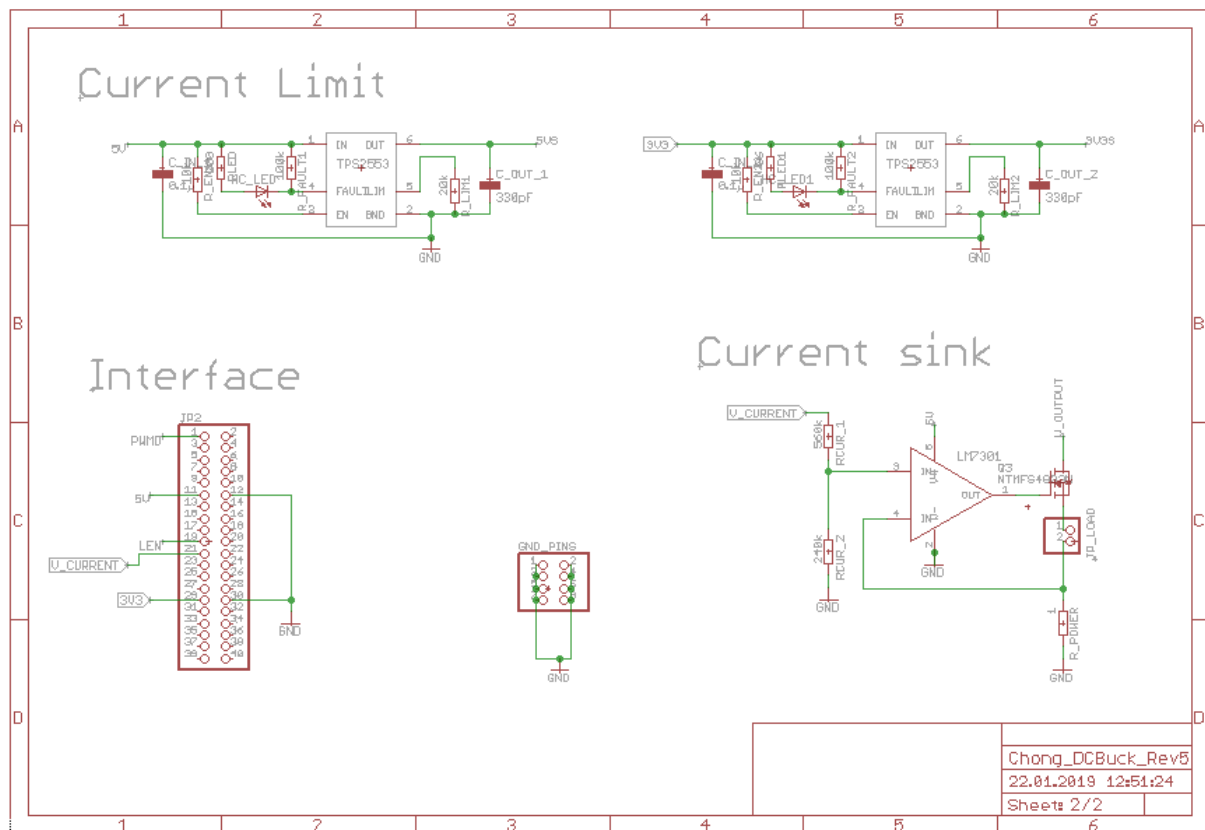


Fig. 2.3: Eagle [18] schematic views of the DCDCbuck Rev. 5 board, by K.-L- Chong [19].

Fig. 2.1 shows the *DEI-SoC* board (left) with plugged-in *DCDCbuck* daughter board (right). The orange wire connects the *DCDCbuck* board's output voltage with the ADC *LTC2308*'s input channel 0 (lower left pin), whereas the *LTC2308* is on board of the *DEI-SoC*.

Fig. 2.2 illustrates the layout of the *DCDCbuck* board with top metal layer brown, bottom metal layer blue and contacts / vias green. (Vias connect different metal layers.)

Fig. 2.3 is the schematic part of (a) the main circuit, and (b) 3.3V and 5V current limiter, interface to *DEI-SoC* board and current sink.

3 DCDCbuck Board

 


Fig. 3.0: DCDCbuck board setup for first tests.

3.1 Starting DCDCbuck Board

Starting with DE1-SoC and DCDCbuck Hardware

Plug daughterboard DCDCbuck into user header JP2 (=gpio_1) of DE1-SoC board (Fig. 3.0).

On the DCDCbuck daughter board:

- Connect cable (orange in Figs. 2.1 and 3.0) from DCDCbuck board's pin ADC_SIGNAL to DE1-SoC board's user header ADC CON, left lower pin (Fig. 2.1).
- Set jumper 3V3 (blue in Fig. 3.0) to supply the daughter board with 3.3V. If a red LED lights up, then the current limiter was activated by a current peak. You will have to unplug the DCDCbuck daughter board or switch off DE1-SoC board to reset the current limiter.
- Set jumper JP_Buck (red in Fig. 3.0) to get a current path to the output.
- Set jumper JP_Load (green in Fig. 3.0) to enable the load current circuitry.
- Set jumper 680uF (brown in Fig. 3.0) to connect the load capacitor
- No need but nice to have for better efficiency: Set jumper Async (pink in Fig. 3.0).

Starting with *Quartus II* Software

Use *Quartus II 18* or later to program *DE1-SoC* board with file *ci_de1soc_DCDCbuck.sof*, that you will get from your supervisor.

- Set switches of the *DE1-SoC* board to $sw(9:0) = "0101\ 00\ 11\ 00"$.
- Get file *ci_de1soc_DCDCbuck.zip* and extract it into directory $...\backslash ci_de1soc_DCDCbuck$. Contains is subdirectory $.\backslash output$ with files $*.cdf$ and $*.sof$.
- Within directory $...\backslash ci_de1soc_DCDCbuck$ click on file *ci_de1soc_DCDCbuck.qpf*. *Quartus II 18* (or later) should start with the actual directory as working directory.
- Select from *Quartus II* main menu: *Tools > Programmer*. The programmer window should open with *Hardware setup...* window showing string *DE1-SoC [USB-1]*. Otherwise, look at *Getting Started with DE1-SoC Board* from the author or any other source to get it running.
- Click on programmer's button *Start* to program the FPGA. You should see a reaction at the LEDs.

Starting the Board

On the 7seg- display, you should see something like "i 1200", which is the set point in millivolts (mV). Set $sw(3) = 0$. You should now see output voltage the measured by the ADC indicated on the 7seg display like "U_1xxx" with xxx being close to 200.

Got it running? Congratulations! You got the board working!

Using the Oscilloscope

Look at the author's document *Quickstarting_DSoX2024_Oscilloscope.pdf* to handle the *DSO-X2024* oscilloscope. In the following, to connect "channel #" stand for: connect the red end of the BNC cable to # and the black end to ground. As can be seen from Fig. 2.1, there is a group of 2x4 ground pins to the right of label "100 μ F" near to the big blue load resistor. In Fig. 3.0 four black ends of BNC-cables are plugged onto these 8 pins, so that some of them cannot be seen in this figure.

Interconnections to the *DSO-X 2024* oscilloscope:

- PWM signal: Connect oscilloscope's channel 1 (**CH1, yellow**) to *pin 1* (upper left) of user header *gpio_0*. (We use $JP1 == gpio_0$, as $JP2 == gpio_1$ is occupied by the DCDCbuck board. *VHDL* statement " $gpio0 \leq gpio_1$ " copies user header *gpio_1* to *gpio_0*.)
- Load: Connect **CH2 (green)** of the oscilloscope to the right jumper pin on the right side of jumper *JP_LOAD (green)*. I shows the voltage at the 1 Ω load resistor, typically 0 or 1V.
- Connect **CH3 (blue)** of the oscilloscope to pin 3 (below pin 1, see -> Fig. 3.0) of user header *gpio_0* of the *DE1-SoC* board.
- Output voltage: Connect **CH4 (red)** of the oscilloscope to pin labeled *OUT* of the *DCDCbuck* board.

Oscilloscope *Auto Scale*

- Switch CH1, CH2, CH3, CH4 of the oscilloscope on. Then press hardkey *Auto Scale*.
- The screen will show an image similar to that of Fig. 3.1(a).

Triggering

- The oscilloscope triggers now the rising edge of **CH1 (yellow)**, indicated by the little yellow triangles at the top and left edge of the screen.
- **CH1 (yellow)** shows the output of the pulse-width modulating (PWM) DAC.
- Push switches $sw(9:6)$ to "1111". Then the PWM-DAC outputs 1's only and the oscilloscope has no more edge to trigger.
- Change the setting of your oscilloscope such, that it triggers **CH3 (blue)**. Now you should have a fixed scope image again.
- It is not wise to scarify a valuable input channel for a simple trigger signal. Consequently:
- Disconnect the BNC cable from **CH3**, plug it at the backside of the scope to external trigger in (*EXT TRIG IN*).
- Switch OFF CH3 of the scope (pressing 1 or 2 times on the respective button at the scope).
- At your scope, select trigger channel external (*EXT*).
- Press *HK AutoScale*. You should now get a standing image on the oscilloscope again.
- Set $sw(9:6)=1000$ and Press *AutoScale*. You should get an image similar to Fig. 3.1(b).

Observing Some Effects

Disconnect all 4 black ground ends from the measurement cables from the ground pins on the DC/DC board to observe the impact of grounding. You should see significantly more voltage overshoot on the oscilloscope. Then connect ground cables again.


Push switch $sw(1) = 1$ corresponding to $LEN = '1'$. Output voltage should remain the same but PWM pulses become a little bit wider. Ok? Set back to $LEN = '0'$ setting $sw(1) = 0$.

Set $sw(0) = 1$. Output voltage should remain the same but pulses become wider. And you can feel with your finger tip that the big blue resistor next to the green jumper will get warm after some seconds? **Green** line in Fig. 3.1 jumps to 1V. Reset load current to zero with $sw(0)=0$.

Saving the Scope's Screen to a File

- Save the screen on a USB memory stick. It must be FAT32 formatted.

(a) Oscillogram showing 4 channels

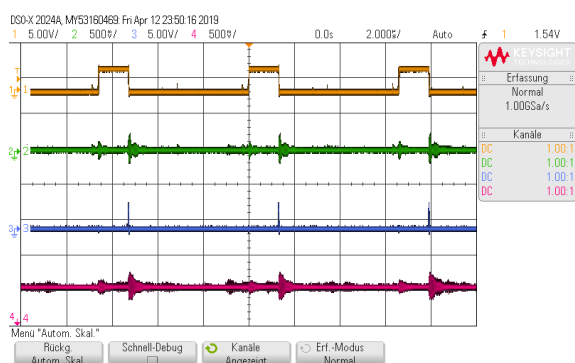

(b) Oscillogram showing 3 channels



Fig. 3.1: Osci screen copies: **CH1 (yellow)**: pulse-width modulated input signal. **CH2 (green)**: voltage at 1Ω load resistor, **CH3 (blue)**: synchronization signal, **CH4 (red)**: output voltage.

3.2 The System Setup

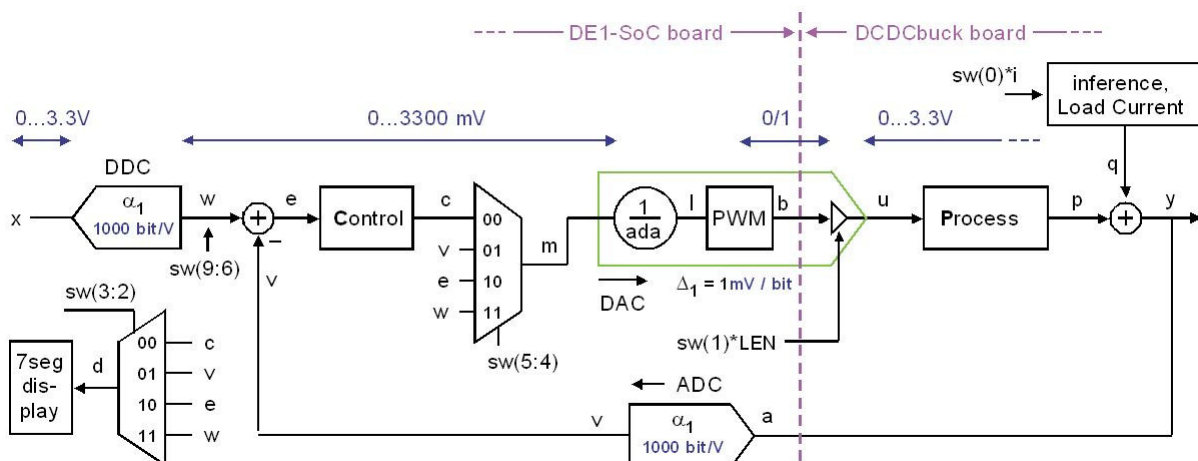


Fig. 3.2: The DC/DC buck converter schematic.

Fig 3.2 illustrates the system with its 2 number ranges:

1. Physical voltage range being mainly defined by the two output voltage levels U_{low} , U_{high} of the PWM DAC. Fig. 3.1 shows example voltages $U_{low} = 0.0V$, $U_{high} = 3.3V$ in blue letters.
2. ADC output range computed as $N_{ADCout} = \alpha_1 \cdot U_{ADCin} + \alpha_0$, with $\alpha_1 = 1000\text{bits/V}$, $\alpha_0 = 0V$ given by ADC *LTC2308* with output range 0...4095 corresponding to 0...4.095V. Consequently, v , w and e are given in millivolts (mV) and voltage range $0...3.3V$ corresponding to integral number range $0...3300$. (To compute input w from x the amplification of the ADC in the feedback branch must be compensated for by the preceding digital-to-digital converter (DDC) with same gain α_1 as the ADC.)

Factor ada is shown as a part of the PWM DAC in Fig. 3.2. It compensates for different amplification of ADC and DAC, so that a direct series of these modules delivers an amplification of 1.

In detail: The PWM DAC with input level l in Fig. 3.2 translates a series of $0 \dots pwm_period$ ones within a period of pwm_period bits into voltage range $U_{low} - U_{high}$. Consequently, its amplification is $\Delta_1 = (U_{high} - U_{low}) / pwm_period$. In the example of Fig. 3.1 with $pwm_period = 330$ this corresponds to a DAC input level range of $l = 0 \dots pwm_period$ resulting in $l = 0...330$. Thus, one bit of DAC input level l corresponds to $\Delta_1 = 10mV$ of DAC output voltage u .

Seven-segment display, switch $sw(3:2)$

Signals c , v , e and w can be selected by switches $sw(3:2)$ to be shown on the 7-segment display in millivolt. Controller output c must be multiplied with $ada = \alpha_1 \cdot \Delta_1 = 10$ to be displayed in mV.

System operation mode, switch $sw(5:4)$

Signals c , v , e and w can be selected by switches $sw(5:4)$ to be fed to the PWM DAC. Signals v , e and w must be divided by $ada = \alpha_1 \cdot \Delta_1$ to deliver a DAC output voltage range of $U_{low} \dots U_{high}$, whereas $U_{low} = 0.0V$, $U_{high} = 3.3V$, $ada = 10$ in the blue example of Fig. 3.1.

User Headers (according to listing 3.2)

- *pwm0* is the pulse-width modulated output signal. Max. number of bits is *pwm_period* which is by default 330, so that 3.3V are set by 330 bits → resolution 10 mV/bit.
- *enc* is a flag having a width of $T_{clock}=20\text{ns}$ used as sync signal for the oscilloscope.
- *LEN* (= Low-side switch ENable) dis-/enables the low-side switching field effect transistor (FET) when 0/1.
- *Iload_ON* switches a load current of $I_L = 1\text{A}$ on when *Iload_ON* = 1.
- *gpio_0* <= *gpio_1*: As user header *JP2* (= *gpio_1*) is covered by the *DCDCbuck* board, this *VHDL* statement copies all signals from *JP2* to free *JP1*, where they can be observed.

Listing 3.2: VHDL code lines of module *deIsoc_DCDbuck(rtl_deIsoc_DCDCbuck)*

```
-- DCDCbuck Daughter Board
gpio_1(0)  <= pwm0;      -- PIN01 = PWM output
gpio_1(2)  <= enc;      -- PIN03 = PWM enable out = contoller enable
gpio_1(16) <= LEN;     -- PIN19 = LEN (=Low driving FET Enable)
gpio_1(18) <= Iload_ON; -- PIN21 = LoadCurrent_ON
-- miscellaneous
gpio_0 <= gpio_1; -- this line delivers more measurement points on gpio_0
```

Table 3.2: Functionality of switches $sw(9:0)$ and push buttons $key(3:0)$

9	8	7	6	5	4	3	2	1	0
Set point $w=1000 \cdot x$ in mV				DAC inp sel		7seg in sel		LEN	i_{Load}

Switches	
sw(9:6)	Select set point x in V
0000	Set point $w = 0$
0001	Set point $w = 250$
0010	Set point $w = 500$
0011	Set point $w = 750$
0100	Set point $w = 1000$
0101	Set point $w = 1250$
0110	Set point $w = 1500$
0111	Set point $w = 1750$
1000	Set point $w = 2000$
1001	Set point $w = 2250$
1010	Set point $w = 2500$
1011	Set point $w = 2750$
1100	Set point $w = 3000$
1101	Set point $w = 3250$
1110	Set point $w = 3500$
1111	Set point $w = 3750$
sw(5:4)	Select quantity fed to the input of the PWM DAC
00	control mode => output c
01	control mode => output v
10	control mode => output e
11	control mode => output w
sw(3:2)	Select quantity displayed on 7-segment display
00	display c in mV
01	display v in mV
10	display e in mV
11	display w in mV
sw(1)	Low-side driver ENable
0	Asynchronous mode: Low-side power-MOSFET is always off.
1	Synchronous mode: Low-side power-MOSFET operates invers to high-side driver
sw(0)	Load current switch
0	Load current OFF
1	Load current of 1A ON

Keys	(=push buttons)
key(0)	Global asynchronous reset, dominant over all other signals: all flipflops are reset to their reset-states
key(1)	Global enable: flipflops do no more change state when key(1) is pushed
key(2)	Load current ON: pushing key(2) has the same effect as $sw(0)='1'$, current flow stops when key(2) is released.
key(3)	hold 7-segment display: 7seg-display is frozen while key(3) is pushed

3.3 Observing DCDCbuck Board Operation Details

3.3.1 DCDCbuck Board: Process and Load current Inference Realization

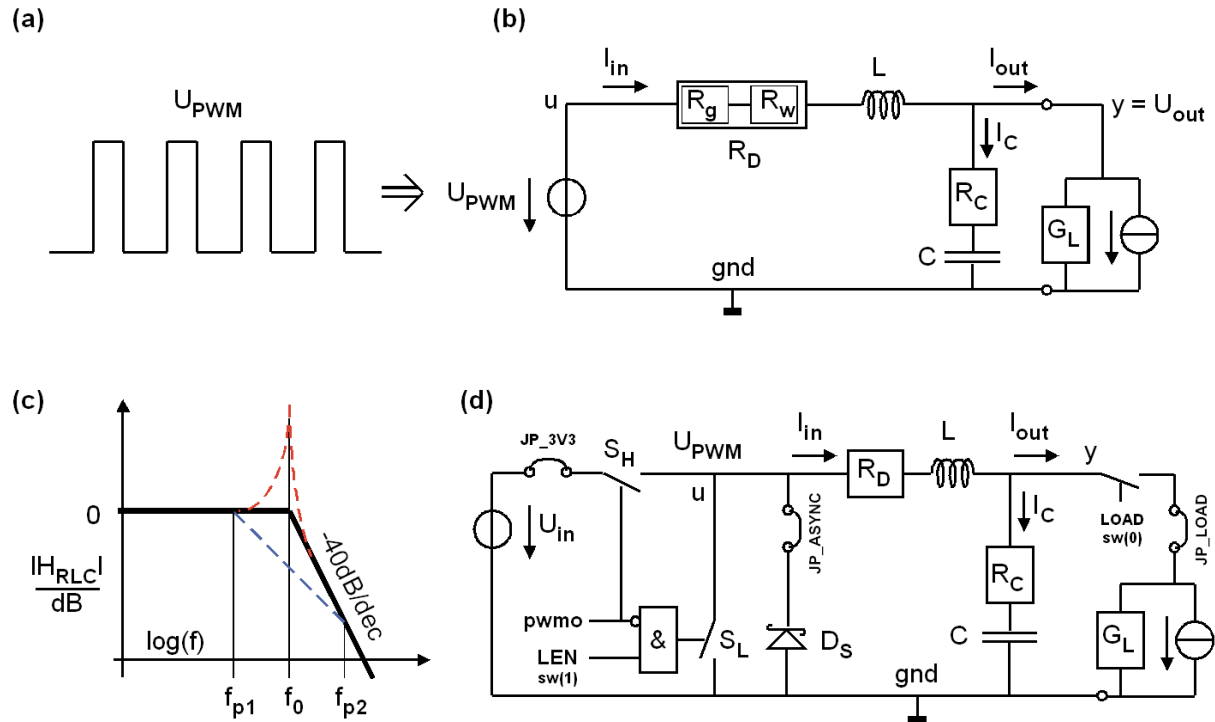


Fig. 3.3: Detailed view of process and load current inference of Fig. 3.2: **(a)** pulse-width modulated input voltage (U_{PWM}), **(b)** smoothed by an LC lowpass damped by some resistors, delivering **(c)** a transfer function over frequency f , and **(d)** is a more detailed view of part (b).

Fig. 3.3 details the boxes illustrated as *process* and *inference load current* in Fig. 3.2:

- (a)** Shows a pulse-width modulated input voltage (U_{PWM}) which is smoothed by an
- (b)** LC lowpass with unavoidable resistors R_D consisting of generator impedance R_g and wire resistance R_w , an equivalent serial resistor (R_C) of the capacitor and load conductance G_L . These resistors effect the damping of the LRLC lowpass, that is illustrating in the
- (c)** Bode diagram, showing asymptotes (**bold solid line**) over frequency f , with oscillating case indicated as **red dashed line** and aperiodic case shown as **blue dashed line**.
- (d)** Is a more detailed view of Fig. part (b), showing jumpers JP_{3V3} , JP_{ASYNC} and JP_{LOAD} being set. Consequently U_{PWM} oscillates between 0V and 3.3V, Schottky diode D_S is ready for supporting asynchronous operation enforced $sw(0)$ setting $LEN = 0$, and a *load current inference* of 1A can be imposed setting the $LOAD$ switch $sw(1) = 1$.

High-side switch S_H and low-side switch S_L are controlled by the digital logic signal $pwm0$ generated by the *FPGA*. A particular chip named *LM27222* [20] makes sure that S_H and S_L are operated non-overlapping, i.e. they never conduct at the same time, because this would open a direct current path from U_{in} to ground.

3.3.2 Operating the *DCDCbuck* Board

Set the set point for the output voltage to $w = 1500\text{mV}$ and observe pulse with of *pwm0*, output voltage U_{out} and voltage over the 1Ω load resistor to know the current.

3.3.2.1 Uncontrolled Operation

We will now use fixed pulse-width for *pwm0* without control:

- Set *control mode* => *output w*.
- Load current off: $sw(0) = LOAD \rightarrow 0$.
- Set synchronous mode: $sw(1) = LEN \rightarrow 1$.
- Show $w = 1500\text{mV}$ on the 7-segment display, then switch to show v , which is measured by the ADC (*LTC2308*).

If we have pulses of $0/3.3\text{V}$, the output voltage of the buck converter should be close to 1500mV .

Switch the load current on. The pulse-width should stay the same and the output voltage should drop by ΔU_{out} , typically some 200mV . This is helpful to compute R_D in Fig. 3.3(d) according to $R_D = \Delta U_{out}/I_{Load}$. What do you measure?

With load current ON, switch to the asynchronous mode. Switch S_L stays always open now. There should not be much change in the output voltage, except that we lose some more energy at the Schottky diode D_S , which is visible as a further output voltage drop.

Now switch the load current OFF. The output voltage begins to rise uncontrolled. This is because there is no more means available to pull U_{out} down: S_L is out of operation, no output current and Diode D_S is reverse biased.

3.3.2.2 Check Controlled Operation Roughly

We will now use adaptively controlled pulse-width for *pwm0*:

- Set *control mode* => *output c*.
- Load current off: $sw(0) = LOAD \rightarrow 0$.
- Set synchronous mode: $sw(1) = LEN \rightarrow 1$.
- Show $w = 1500\text{mV}$ on the 7-segment display, then switch to show v , which should be close to 1500 .

Check output voltage roughly with and without load current, synchronous and asynchronous operation. The controller should now adapts the pulse-width on signal *pwm0* such, that the output voltage keeps constantly at some 1500mV .

3.3.2.3 Controlled Operation in Continuous Mode

For continuous mode, switch load current ON. Current through the inductor and low-side switch S_L is always in the same direction.

We now have the situation that output voltage is controlled by adapting pulse width. Less pulse-width at same output voltage and current corresponds to more efficiency.

Switch between synchronous and asynchronous mode: Enable and disable low-side switch S_L using $sw(1) = LEN$. We see, that the converter operates more efficient (pulses are narrower) with $LEN=1$ as voltage drop across conduction switch S_L is less than through diode D_S .

Remove/set jumper JP_ASYNC several times to enable/disable diode D_S . We find that efficiency without D_S is lower but the circuit still works well, because low-side switch S_L has a built-in silicon diode. Schottky diode D_S has some 0.2V less forward voltage drop being more efficient and preventing switch S_L from heating.

3.3.2.4 Controlled Operation in Discontinuous Mode

For discontinuous mode, switch load current OFF. Current through the inductor and low-side switch S_L will now oscillate back and forth.

We still have the situation that output voltage is controlled by adapting pulse width and that less pulse-width at same output voltage and current corresponds to more efficiency.

Switch between synchronous and asynchronous mode: Enable and disable low-side switch S_L using $sw(1) = LEN$. We see, that the converter operates more efficient (pulses are narrower) with $LEN=0$. This is because the operating low-side switch S_L (in sync mode) pulls inductor current into inverse direction and leads it to ground. This is prevented in asynchronous mode by the diode. In the uncontrolled mode output voltage would rise uncontrolled, however, now in controlled mode pulse-width at signal $pwmo$ is reduced to keep output voltage on a correct value.

Consequently, in cases of discontinuous operation due to low load currents the circuit operates more efficiently in the asynchronous mode.

3.4 Getting Along with the Digital Part

3.4.1 Load Current Sink

Read this carefully to not destroy the DCDCbuck board!

Avoid long phases of load current flow, particularly with high output voltages!

Setting $sw(0)=1$ or pressing push button $key(2)$ turns the load current on, when jumper JP_Load (green in Fig. 3.0) is set to allow for load current flow.

Experiment: Set output voltage (labeled y in Fig. 3.2) to $U_{out} = 1.2V \Leftrightarrow sw(9:6) = "1000"$. Turn load current on $\Leftrightarrow sw(0) = '1'$ (or $key(2)$ pushed) and “measure” with your finger tip how load resistor R_L (labeled R_POWER on the DCDCbuck board) becomes warm.

Load resistor R_L has to translate a maximum of $P_L = I_L \cdot U_L = 1A \cdot 1V = 1W$ of electrical power to thermal heat. This will mostly be done by transferring heat to surrounding air molecules.

The significantly smaller power FET (the “big” black square right to R_POWER) has to translate the rest of the load current’s energy to thermal heat, that is $P_{FET} = I_L \cdot (U_{out} - 1V)$. This is performed by transferring heat to surrounding air molecules and to the board. Take care! **We have already “killed” several of those power FETs!**

For an output voltage of $x V$, we have a total load power of $1A \cdot xV = x W$. The load resistor R_L translates $1W$ to thermal heat. The (smaller) power FET has to dissipate the remaining $(x-1) W$. If you tip your finger on the power FET to feel how it becomes hot, please do not touch its metal contacts as remaining salt of your fingers will cause leakage currents.

Exercise: Let $U_{out} (= y) = 2.7V$ and load current on: $I_L = 1A$. What is the total load power that must be translated to heat, and witch power shares are dissipated by R_L and the power FET?

Total load power $P_{L,tot} =$

 Resistor’s power dissipation $P (R_L) =$

 FET’s power dissipation $P (FET) =$

Functionality of the load current circuitry (Electronics students only)
 Look at *Current Sink* schematics in Fig. 2.3 or download Eagle files *DCDCbuck_Rev5.sch* and *~.brd* from the author. Both $sw(0)$ and pushing $key(2)$ will drive the wire labeled $V_CURRENT$ from logic '0' (0V) to logic '1' (3.3V). The non-inverting input voltage (pin 3) of operational amplifier (OA) *LM7301* gets 1/3 of this voltage, so that the pin 3 toggles between 0 and 1V. OA *LM7301* will do anything it can to get its inverting input (its pin 4) to the same voltage as pin 3. This can be achieved when $U_{out} \geq 1.2V$. As the voltage at pin 4 is the voltage at the load resistor, $R_L=1\Omega$, the load current is controlled to $I_L = 1V/1\Omega = 1A$.

Solutions to the exercise above:

Total load power $P_{L, tot} = I_L \cdot U_{out} = 1A \cdot 2.7V = 2.7W$
 Resistor's power dissipation $P(R_L) = I_L \cdot U(R_L) = 1A \cdot 1V = 1W$
 FET's power dissipation $P(FET) = I_L \cdot U(FET) = 1A \cdot (U_{out} - 1V) = 1.7W$

3.4.2 Testing the PWM DAC

With jumper settings as explained in chapter 3.0 and shown in Fig. 3.0, do the following switch settings (whereas "<=" is a VHDL signal driver):

- Set switches to: $w=1200$ [mV], pulse width: $l = w/ada$, $sw(9:0) =$
 7-weg display shows w , $LEN=0$, Load current OFF
 (solution see next page).
- In this mode the pulse-width is constant, whatever happens to the output voltage.
- Set point: $w = 1200$, corresponding to 1200mV when *DCDCbuck's* $V_{CC}=3.3V$.
- PWM DAC gets level $l \leq w/ada$ to translate set point w into mV of output voltage.
- 7-segement display gets $d \leq w$ to display set point (input) "**i 1200**".
- Synchronous mode on $\Leftrightarrow LEN='1'$ (Low-side switch ENabled)
- Load current off.

You should now see the set point $w = 1200$ on the 7-segment display as string "**i 1200**".

- Switch displayed voltage to $l \leq v$, displaying output voltage y as measured by the ADC.
- Displayed voltage should be around 1200 [mV].
- Compare v to output voltage y measured by CH4 of the oscilloscope. Should be similar.

Synchronous Mode Off $\Leftrightarrow LEN \leq 0$.

Output voltage y will now float up, because positive PWM pulses pump charges on the load capacitor while there is no way to discharge them again, as Low-side switch Enable (LEN) is 0 and the pull-down FET doesn't operate any more.

For electronics students: Current flowing out of the inductor's right side must flow in on its left side, also when the high-side switch is open. This is why we need the diode enabled with jumper labeled *Async* on the *DCDCbuck* board (pink jumper in Fig. 3.0). The Schottky diode is efficient but dispensable, as the deactivated power FET has an unavoidable build-in diode. However, it is not very efficient due to a high flow voltage, as the power FET are not optimized to operate as diodes. The difference may be 200mV flow voltage, not much but important to obtain high DC/DC conversion efficiency in asynchronous operation.

Load Current On

Within asynchronous mode of operation switch Load current on. Now the capacitor can be discharged over the load current and the output voltage falls some 100mV under the set point.

3.4.3 Testing Closed Loop DC/DC Buck Conversion Mode

Set switches to feed controller output c to the PWM DAC input l while *DCDCbuck* output voltage is fed back to the ADC, channel 0 (lower left pin of header *ADC CON*), 7-seg showing w , $LEN=1$, load current off:

$sw(9:0) =$ (solution at the end of this page)

Now the pulse width should be automatically adopted to hold the output voltage constant, whatever load condition we have. you should see w indicated as "**i 1200**" on the 7-segment display.

Toggle $sw(3)$ to $sw(3)=0$. Now the 7-seg displays should show process variable v which is the *DCDCbuck*'s output voltage in mV as measured by the ADC.

Check this for different settings of set point w , synchronous and asynchronous mode, with and without load current. Does the system hold the output voltage constant? Should!

3.4.4 Testing the ADC

Set the output of your wave generator (oscilloscope output *WaveGen*) to DC, 2V and connect it (i) to a free channel on your oscilloscope and (ii) to the ADC input channel 0 (lower left pin of header *ADC CON*). Further set $sw(3:2)$ to $sw(3:2)="01"$, so that the 7-segment display shows the voltage of the *WaveGen*. Change output voltage of Wavegen in the range of 0...5V and compare the voltage measured with the oscilloscope and with the ADC. They should be very similar! Measure DC voltage of you oscilloscope with the **measurement** menu.

Solution to 3.3.2 initial setting: $sw(9:0) = 1000\ 11\ 11\ 00$
Solution to 3.3.3 initial setting: $sw(9:0) = 1000\ 00\ 11\ 10$

3.5 Characterizing the RLC Lowpass (DC/DC Students only!)

What is your board number?

.....

3.5.1 Measuring Load Capacitors $C_{L\#}$

Measure the load capacitances on the *DCDCbuck* board. In the Electronics Laboratory of OTH Regensburg use *HM8118*.

Table 3.4.1: Load capacitance combinations

Device(s)	Capacitance nominal	Capacitance measured	Equivalent series resistor measured
C_{L1}	100 μF		
C_{L2}	330 μF		
C_{L3}	680 μF		
$C_{L1} + C_{L2}$	430 μF		
$C_{L1} + C_{L3}$	780 μF		
$C_{L2} + C_{L3}$	1010 μF		
$C_{L1} + C_{L2} + C_{L3}$	1110 μF		

3.5.2 Measuring Inductors $L_{\#}$

Measure inductance combinations on the *DCDCbuck* board. In the Electronics Laboratory of OTH Regensburg use *HM8118*.

Table 3.4.2: Load inductance combinations

Device(s)	Inductance nominal	Inductance measured	Equivalent series resistor measured
L_1	10 μH		
L_2	33 μH		
$L_1 + L_2$	43 μH		

3.5.3 Measuring Total Series Resistor R_D

Use switches to select constant pulse with and set points according to table 3.4.3. Measure average output voltage U_{out} ($=y$ in Fig. 3.2), e.g. with oscilloscope or with a voltmeter.

Measure output voltage with and without load current and compute the total series resistor R_D from the resulting voltage difference: $R_D = (U_{out|IL=OFF} - U_{out|IL=ON}) / I_L$. Remove jumper JP_Load (green in Fig. 3.0) and replace it by an Ampere meter to get the accurate current.

Table 3.4.3: Total series resistor, measured from $R_D = (U_{out|IL=OFF} - U_{out|IL=ON}) / I_L$.

Set point w	$U_{out IL=0}$	$U_{out IL=ON}$	I_L when ON	R_D
1200				
1800				
2700				

3.5.4 Measuring a Bode Diagram of the RLC Low-Pass

3.5.4.1 Measure Point by Point

Open feedback loop wire between nodes y and a in Fig. 3.2 (orange wire in Figs. 2.1 and 3.0). Set switches to drive ADC output to PWM input, obtaining level $l \leq v/ada$.

Connect DSO-X oscilloscope generator to CH 3 of the oscilloscope. (Other channels as described above: CH1: PWM output, CH2 $V(R_{LOAD})$, CH4 U_{out} ($=y$), probably Ext Trig IN to sync-signal pin3 of JP1.) Set WaveGen output to a DC-Signal of $V_{CC} / 2$ (should be 1.65V).

Feed the 1.65V from the oscilloscope's *WaveGen* output also to the ADC input channel 0 (node a in Fig. 3.2). You should observe that the U_{out} (node y in Fig. 3.2) at CH4 follows U_{in} at CH3. Modify WaveGen output in a range of $V_{CC}/2 \pm 1V$ to verify that.

With offset of $V_{CC} / 2$ (should be 1.65V) set *WaveGen* to add an AC amplitude at node a of $2V_{pp}$ ($=2V$ peak-to-peak), i.e. a sinusoidal wave with swing $V_{CC}/2 \pm 1V$ at 10Hz. Measure output amplitude and phase of y/a and fill the gaps in table 3.4.4.

Table 3.4.4: Points of a Bode diagram

$f / \text{Hz} =$	10 Hz	50Hz	100	500	1000	5000	10000	
$ y/a $ ($ U_{out}/U_{in} $)								0.71
$angle(y/a)$								45°

4 Conclusions

DCDCbuck board was operated as daughterboard of *DEI-SoC* board. Basic digital functionality was tested, *RLC* low pass was characterized. The reader is now ready for modeling and simulation with the parameters obtained.

5 References

- [1] Available: <https://www.terasic.com.tw>.
- [2] Available: <https://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&No=836>
- [3] Available: <http://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&No=886>
- [4] Available: <https://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&CategoryNo=165&No=836&PartNo=4>
- [5] CD ROM *DEI-SoC CD-ROM (rev.F Board) Version 5.1.2 of 2910-01-28* from [4]
- [6] *DEI-SoC* User Manual, Ref. F, taken from [5], available: https://hps.hs-regensburg.de/~scm39115/homepage/education/labs/Lab_ElectronicBoards/DEI-SoC_UserManual.pdf
- [7] *DEI-SoC* Schematic, Ref. F, taken from [5], available: https://hps.hs-regensburg.de/~scm39115/homepage/education/labs/Lab_ElectronicBoards/DEI-SoC_Schematic_revF.pdf
- [8] K:\SB\Sources\EDA\Terasic\Hardware\
- [9] Available: https://en.wikipedia.org/wiki/Intel_Quartus_Prime
- [10] Available: <https://en.wikipedia.org/wiki/ModelSim>
- [11] Av. <https://www.intel.com/content/www/us/en/programmable/downloads/download-center.html>
- [12] Available: <https://edg.uchicago.edu/~tang/VHDLref.pdf>
- [13] Available: https://www.mimuw.edu.pl/~marpe/pul/card_vhdl.pdf
- [14] Available: https://www.mimuw.edu.pl/~marpe/pul/card_1164.pdf
- [15] Available: <https://hps.hs-regensburg.de/scm39115/>
- [16] MAX4230 - MAX4234 data sheet, Maxim Integrated, Available: <https://datasheets.maximintegrated.com/en/ds/MAX4230-MAX4234.pdf>
- [17] LT1711 / 1712 Rail-to-Rail Comparators, Analog Devices (Linear Technology) Available: <https://www.analog.com/media/en/technical-documentation/data-sheets/171112f.pdf>
- [18] *Eagle*, CadSoft Computer GmbH, Available: <http://ftp.cadsoft.de/freeware.htm>.
- [19] Kwang Liang Chong, "*Design, Manufacturing, Optimization and Characterization of a DC/DC Buck Converter Board Driving Up to 30V/4.5A for FPGA and μ C Control*", BA Thesis, OTH Regensburg, Electronics Lab., Feb. 2019.
- [20] Texas Instruments, *LM27222 High-Speed 4.5A Synchronous MOSFET Driver*, available: <http://www.ti.com/lit/ds/symlink/lm27222.pdf>