



# Considering Input and Output Impedances

Martin J. W. Schubert

Electronics Laboratory, Regensburg University of Applied Sciences, Regensburg

# Considering Input and Output Impedances


**Abstract.** This document illustrates how to cope with input and output (I/O) impedances.

## 1 Introduction

### 1.1 Motivation

It is important to consider I/O impedances of instrumentation. The *RLC* oscillator in Fig. 1 for example is typically computed as function of the capacitor's equivalent series resistor and the wire resistor of the coil, represented by  $R_C$  and  $R_w$  in Fig. 1, respectively, which are typically in the range of  $\leq 0.1\Omega$ . Consequently, the dominating resistor in this configuration is the output impedance of the signal source, which is typically  $R_g = 50\Omega$  if a waveform generator is employed. In addition, monitor units may have impact on measured results.

**Fig. 1:** *RLC* oscillator

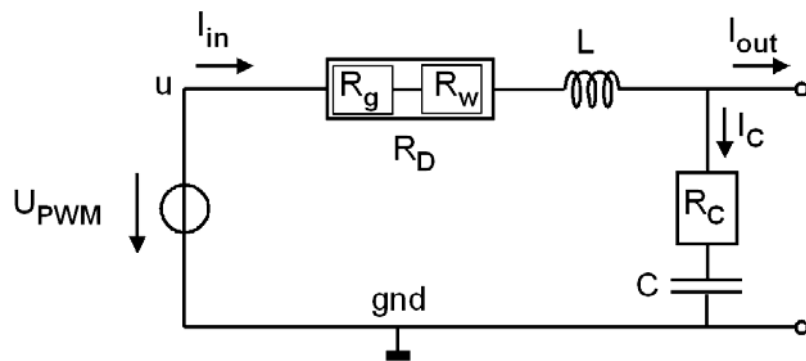

### 1.2 Outline

The organization of this communication is as follows:

- Section 1 introduces into this document
- Section 2 presents fundamental equations
- Section 3 copes with output impedances and
- Section 4 deals with input impedances, while
- Section 5 concludes this document and
- Section 6 offers some references

## 2 Fundamentals


The voltage divider in Fig. 2 delivers for output voltage  $U_o$  and source voltage  $U_s$

$$\alpha = \frac{U_o}{U_s} = \frac{Z_2}{Z_1 + Z_2} \quad (1.1)$$

and consequently

$$Z_1 = \frac{1-\alpha}{\alpha} Z_2 \quad (1.2)$$

$$Z_2 = \frac{\alpha}{1-\alpha} Z_1 \quad (1.3)$$

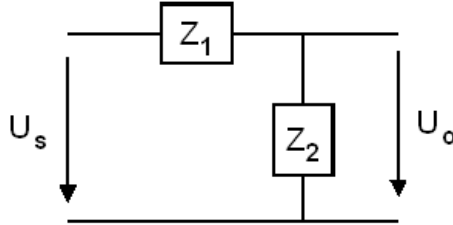

**Fig. 2:** voltage divider

### 3 Measuring Output Impedances

#### 3.1 DC Output Impedance

The voltage divider in Fig. 1 delivers for output voltage  $U_o$  and source voltage  $U_s$

$$\alpha = \frac{U_o}{U_s} = \frac{R_L}{R_o + Z_L} \quad (2.1)$$

and consequently

$$R_o = \frac{1-\alpha}{\alpha} R_L \quad (2.2)$$

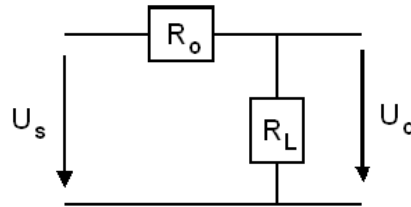


Fig. 3.1: voltage divider

- Step 1: Measure  $U_s$  via  $U_o = U_s$  using  $R_L \rightarrow \infty$ ,
- Step 2: Measure  $U_s$  with a load resistor  $R_L$  with similar size as  $R_o$ ,
- Step 3: Compute  $\alpha$  according to (2.1),
- Step 4: Compute  $R_o$  according to (2.1).

#### 3.2 AC Output Impedance

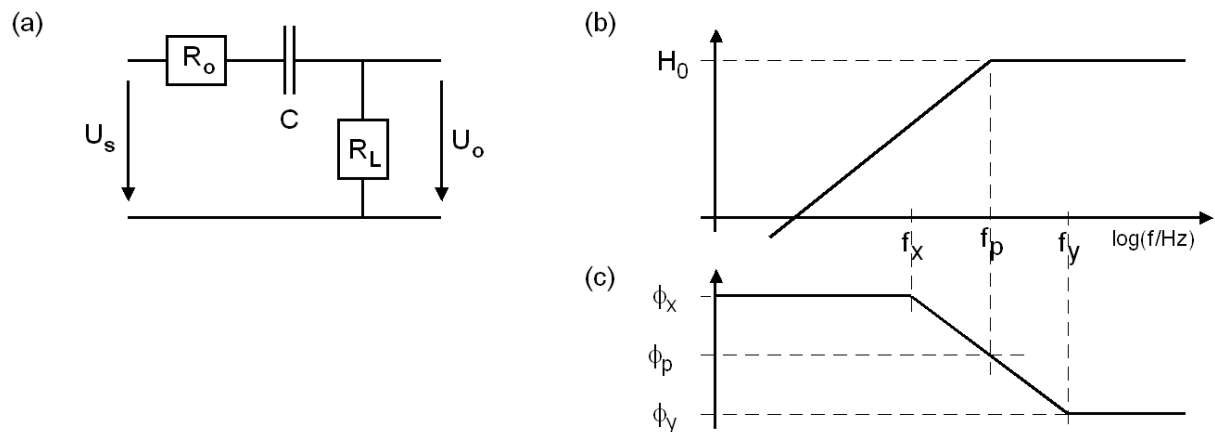


Fig. 3.2: (a) schematic, (b) amplitude- und (c) phase-diagramm.

Its transfer function is

$$H(s) = \frac{U_o(s)}{U_s(s)} = \frac{H_\infty}{1 + s/\omega_p} \quad (2.3)$$

with

$$H_\infty = \frac{R_L}{R_o + R_L} \quad (2.4)$$


and

$$\omega_p = \frac{1}{R_{oL}C} \Leftrightarrow f_p = \frac{1}{2\pi R_{oL}C} \quad (2.5)$$

and

$$R_{oL} = R_o + R_L \quad (2.6)$$

## 4 Measuring Input Impedances

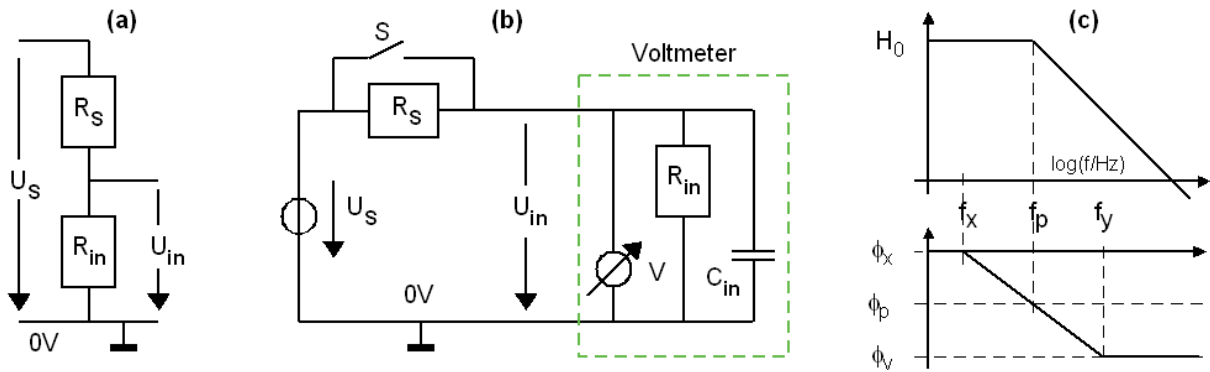

**Fig. 4:** (a) resistive voltage divider, (b), circuit to measure  $R_{in}$ ,  $C_{in}$ , (c) Bode diagram

### 4.1 DC Input Impedance

The Transfer function of the circuit in Fig. 4(a) is

$$H_0 = \alpha = \frac{U_{in}}{U_S} = \frac{R_{in}}{R_S + R_{in}} \quad (3.1)$$

with  $U_S$  and  $R_S$  being the source voltage and shunt resistor, respectively, and  $U_{in}$  input voltage of the voltmeter.  $U_S$  can be measured either with closed switch  $S$  or we simply measure both  $U_S$  and  $U_{in}$ , for example on the two channels of an oscilloscope. The input impedance of the voltmeter can be measured as

$$R_{in} = \frac{\alpha}{1-\alpha} R_S \quad (3.1)$$

### 4.2 AC Input Impedance

The Transfer function of the circuit in Fig. 4(b) with open switch  $S$  is

$$H(s) = \frac{U_{in}}{U_S} = \frac{H_0}{1 + s/\omega_p} \quad (3.2)$$

with

and

$$R_p = R_o \parallel R_L = \frac{R_o \cdot R_L}{R_o + R_L} \quad (3.3)$$

$$\omega_p = \frac{1}{R_p C_{in}} \Leftrightarrow f_p = \frac{1}{2\pi R_p C_{in}} \quad (3.4)$$

The input capacitor of the voltmeter,  $C_{in}$ , can then be computed from

$$C_{in} = \frac{1}{2\pi R_p f_p} \quad (3.5)$$

Step 1: Measure  $R_{in}$  at  $f = 0$  Hz or at least at  $f \ll f_p$ .

Step 2: Compute  $H_0 = \alpha$  and  $R_p$  according to (3.1) and (3.3).

Step 3: Figure out  $f_p$ . At this frequency  $H_0 = 1/\sqrt{2} = 0.707$  and the phase shift is  $45^\circ$ .

## 5 Conclusions

Some simple methods to compute input and output impedances of measurement equipment were presented.

## 6 References

[1] *OTH Regensburg*, available [www.oth-regensburg.de](http://www.oth-regensburg.de)